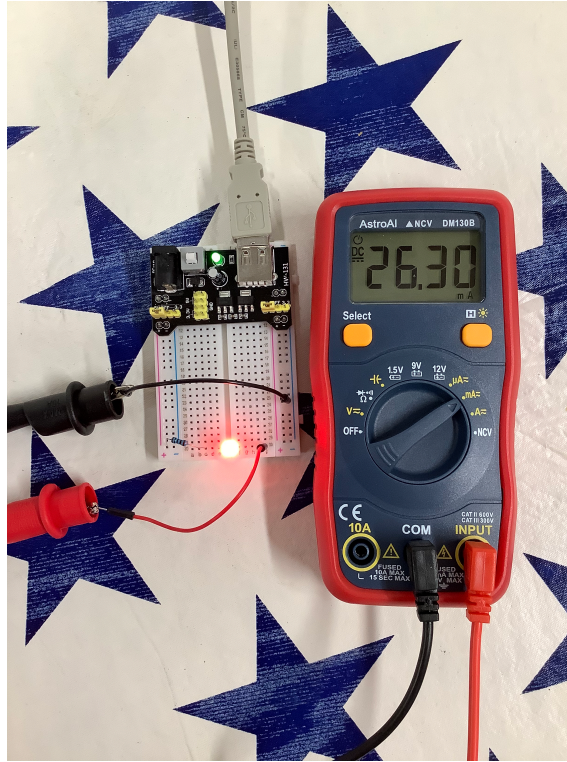



DMM: Fuse Test



Build circuit with LED
and 100Ω resistor



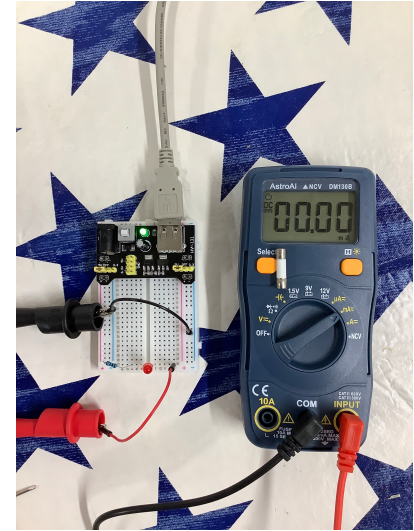Break circuit, insert
Ammeter, read current



With no or bad
Fuse, Ammeter
reads zero and
LED is off