Building a Super-Heterodyne Receiver to Observe the 21 cm Line

Ted Jaeger Advisor : Dr. Robert Mutel



e-SRT Design Goals

- Reduce a 1420.358 MHz (21 cm) signal to 1 MHz (in the center of a 2 MHz window)
- Build a receiver with low System Temperature and amplify the signal by approximately 120 dB
- Create a "Teaching Device" vs. a "Black Box"

System Temperature

- The System Temperature typically has three parts
- \blacksquare Each component (Amplifier, Splitter, etc.) contributes to the Receiver Temperature $T_{\rm R}$

and for multiple Amplifiers ...





Amplification and System Temperature					
Т(К)	G (dB)	Total T _{SYS} (K)	Total Gain (dB)		
3	0.0	3.0	0.0		
50	0.0	53.0	0.0		
13.7	-0.2	66.7	-0.2		
20.7	-0.3	88.4	-0.5		
20.7	-0.3	111.7	-0.8		
27.9	14.0	145.3	13.2		
35.4	-0.5	147.0	12.7		
288.6	23.5	162.5	36.2		
	T(K) 3 50 13.7 20.7 20.7 27.9 35.4 288.6	Figure G (dB) 3 0.0 50 0.0 13.7 -0.2 20.7 -0.3 20.7 -0.3 27.9 14.0 35.4 -0.5 288.6 23.5	Temperature T(K) G (dB) Total T _{SVS} (K) 3 0.0 3.0 50 0.0 53.0 13.7 -0.2 66.7 20.7 -0.3 88.4 20.7 -0.3 111.7 27.9 14.0 145.3 35.4 -0.5 147.0 288.6 23.5 162.5		









Amplification and System Temperature					
Object	т(К)	G (dB)	Total T _{SYS} (K)	Total Gain (dB)	
Front End Box			162.5	36.2	
1st Mixer	1340.8	-7.5	162.8	28.7	
2nd BPF	35.4	-0.5	163.1	28.2	
1st IF1 Amp	288.6	28.0	163.3	56.2	
2nd IF1 Amp	288.8	28.0	163.3	84.2	















Amplification and System						
Temperature						
Object	T(K)	G (dB)	Total T _{SYS} (K)	Total Gain (dB)		
			100 5	00.0		

Front End Box			162.5	36.2	
IF1 Module			163.3	84.7	
2nd Mixer	1340.8	-7.5	163.3	76.7	
3rd BPF	35.4	-0.5	163.3	76.2	
1st IF2 Amp	288.6	28.0	163.3	104.2	
1st IF2 Amp	288.6	28.0	163.3	132.2	