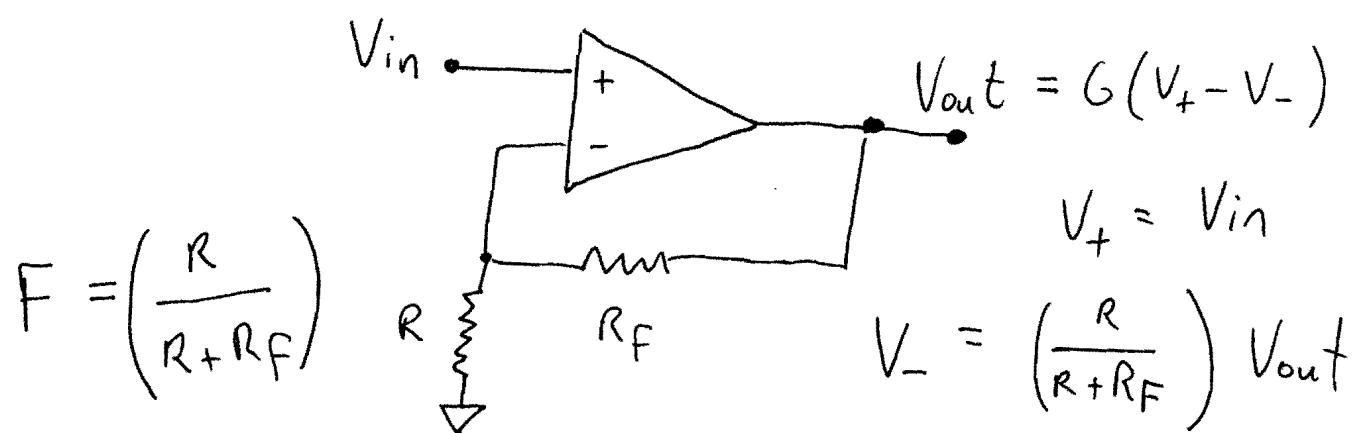


Non-Inverting Amplifier :

The name "non-inverting" is due to the amplified signal which is in phase with V_{in} .




V_- = potential between V_- and ground, which is the same as V_R .

$$V_{out} = G(V_+ - V_-) = G(V_{in} - F V_{out})$$

$$V_{out}(1+GF) = G V_{in}$$

$$V_{out} = \left(\frac{G}{1+GF}\right) V_{in} \approx \frac{1}{F} V_{in} \quad (\text{when } GF \gg 1)$$

①

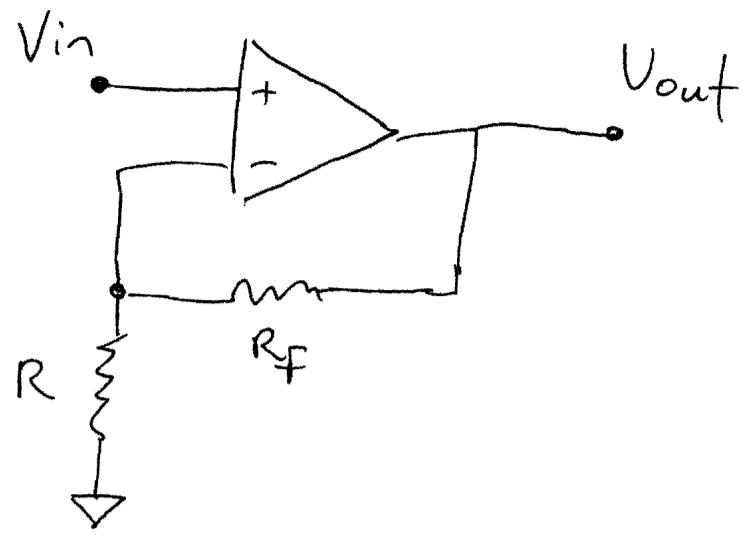

$$V_{\text{out}} \approx \frac{1}{F} V_{\text{in}} = \left(\frac{R + R_f}{R} \right) V_{\text{in}}$$

$$V_{\text{out}} \approx \left(1 + \frac{R_f}{R} \right) V_{\text{in}}$$

Remember that this is the ideal case. Unless you trim the offsets there will be an offset potential V_{off} ($\sim \mu\text{V}$ range)


True signal : ... (almost) ^{minimum}

$$V_{\text{out}} \approx \left(1 + \frac{R_f}{R} \right) (V_{\text{in}} + V_{\text{off}})$$

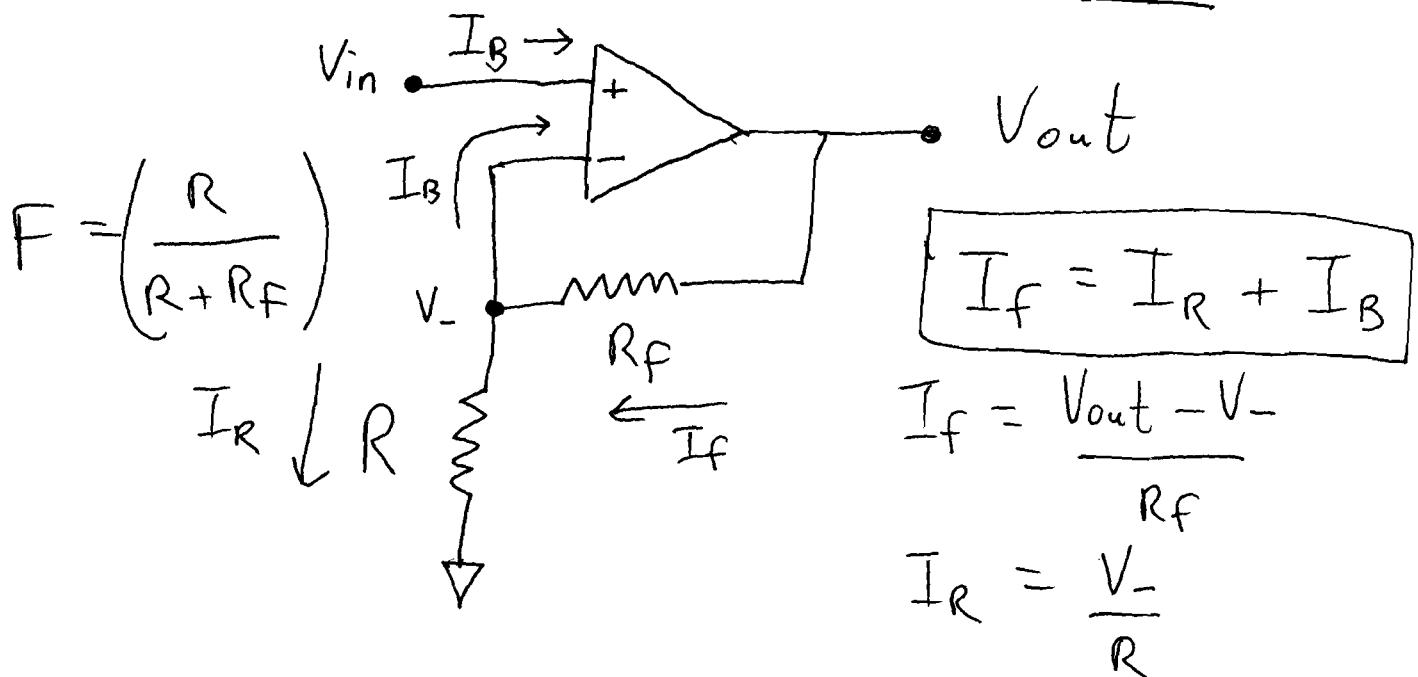(2)

Input Bias Current :

We already discussed the offset potential. There is another non-ideal behavior called Input Bias Current.



$$I_f = I_R + I_B \text{ implies } \frac{V_{out} - V_-}{R_F} = \frac{V_-}{R} + I_B$$

$$\rightarrow V_{out} = I_B R_F + V_- \left(1 + \frac{R_F}{R} \right)$$

$$\text{Now calculate } = \frac{1}{F}$$

$$V_{out} = G(V_+ - V_-)$$

(3)

$$V_{out} = G(V_{in} - FV_{out} + FI_B R_F)$$

$$V_{out}(1+GF) = G(V_{in} + FI_B R_F)$$


$$V_{out} \approx \frac{1}{F} (V_{in} + FI_B R_F)$$

(when GF >> 1)

$$V_{out} = \frac{1}{F} V_{in} + \underbrace{I_B R_F}_{I_B \text{ correction}}$$

Real Total Picture :


"offset potential"

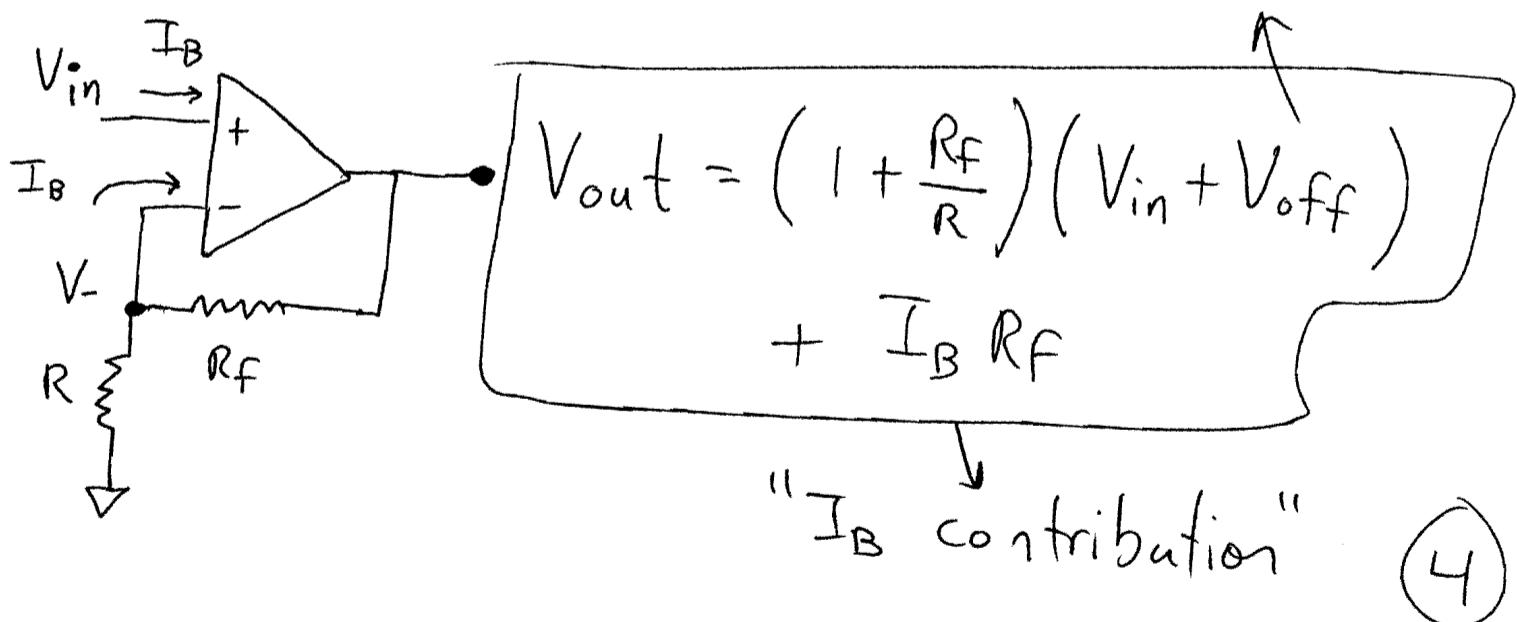

Correction For I_B :

Recall to fix V_{off} we use a potentiometer. How do you fix the I_B correction?

$$I_B = \frac{(V_{in} - V_+)}{R_3}$$

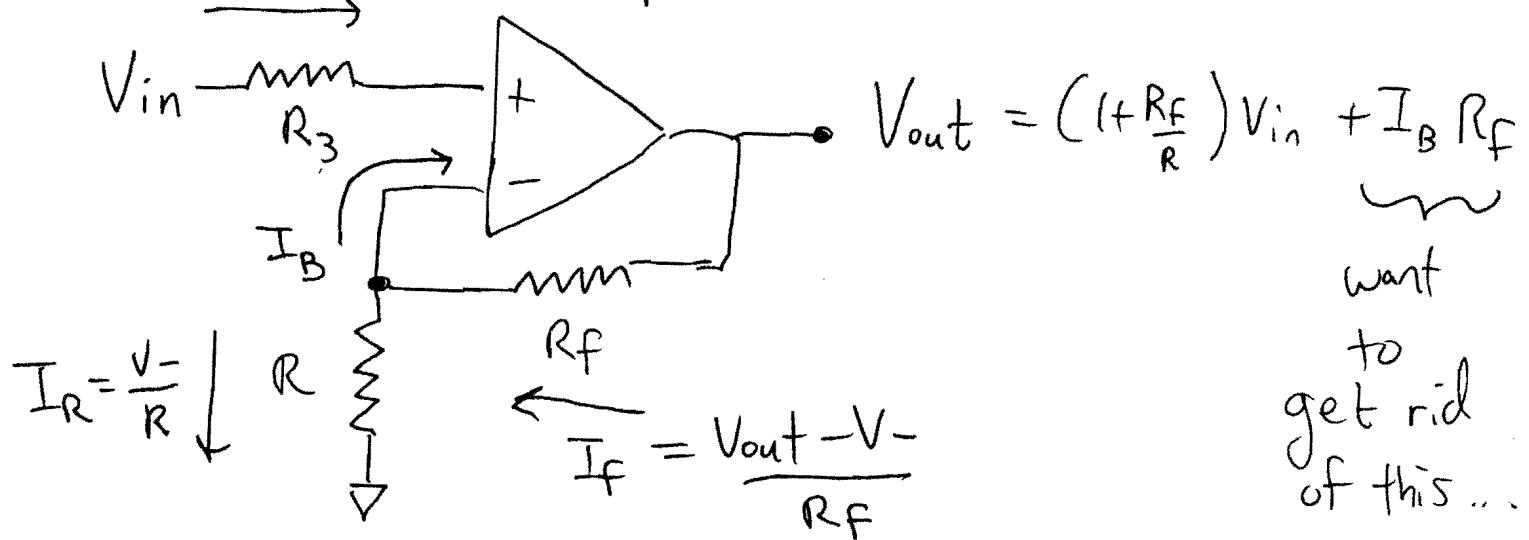

Solution :
$$\boxed{R_3 = R_f \parallel R = \frac{RR_f}{R+R_f}}$$

Proof :
$$I_B = \frac{(V_{in} - V_+)}{R_3},$$

Therefore $V_{in} = I_B R_3 + V_+$

(5)

$$V_{in} = I_B R_3 + V_+ = \frac{I_B R_F}{\left(1 + \frac{R_F}{R}\right)} + V_+$$

$$F = \frac{R}{R+R_F} ; \quad \frac{1}{F} = \left(1 + \frac{R_F}{R}\right)$$

(1)

$$V_+ = V_{in} + -F I_B R_F$$

$$\text{Use } I_B + I_R = I_f$$

$$I_B + \frac{V_-}{R} = \frac{V_{out} - V_-}{R_F}$$

(2)

$$\Rightarrow V_- = F V_{out} - I_B R_F F$$

Combine (1) and (2)

and compute $V_{out} = G(V_+ - V_-)$

(6)

$$V_{out} = G(V_+ - V_-) = G \left[V_{in} - F I_B R_f - (F V_{out} - I_B R_f F) \right]$$

$$V_{out} = G[V_{in} - F V_{out}]$$

$$V_{out} \approx \frac{1}{F} V_{in}$$

or

$$V_{out} = \left(1 + \frac{R_f}{R}\right) V_{in}$$

when

$$R_3 = R_f \parallel R = \frac{R_f R}{R_f + R}$$

(7)