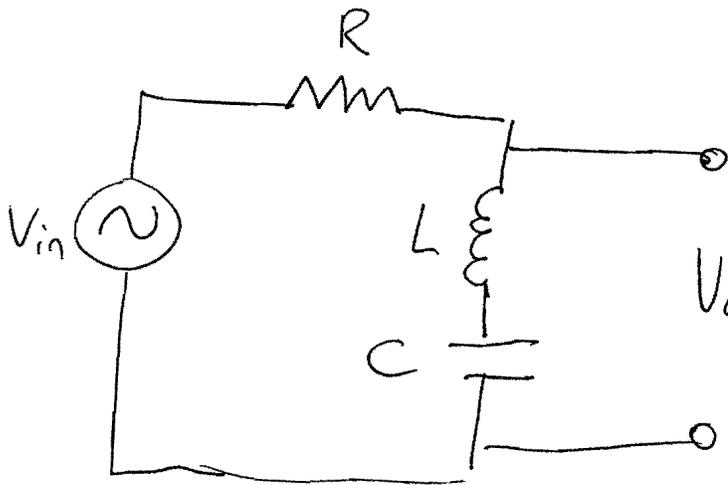


RLC Frequency Response:


(1)

Series Circuit:




$$V_{out} = \left(\frac{z_L + z_C}{z_L + z_C + R} \right) V_{in}$$

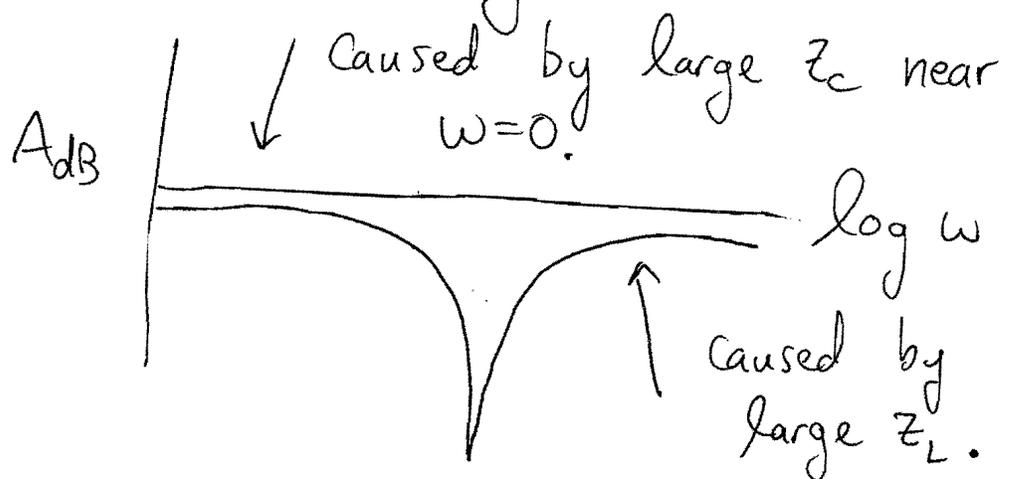Remember that high impedance across the circuit element that you're measuring from will result in large V_{out} . Therefore, the circuit above is a notch filter (when measuring from the LC.)



Series RLC transmission function (2)

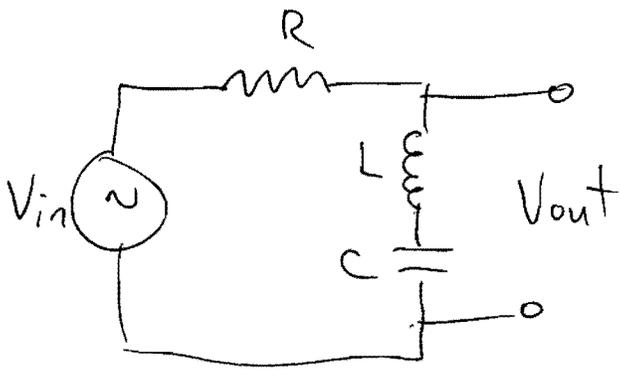

$$A(\omega) = \frac{Z_L + Z_C}{Z_L + Z_C + R}$$



$$A(\omega) = \frac{(i\omega L + \frac{1}{i\omega C})}{(i\omega L + \frac{1}{i\omega C}) + R} = \frac{1}{1 + \frac{R}{i(\omega L - \frac{1}{\omega C})}}$$

$$A(\omega) = \frac{1}{1 - \frac{iR}{(\omega L - \frac{1}{\omega C})}}, \quad \text{put in polar form.}$$

$$A(\omega) = \frac{e^{i \tan^{-1} \left(\frac{R}{\omega L - \frac{1}{\omega C}} \right)}}{\sqrt{1 + \left(\frac{R}{\omega L - \frac{1}{\omega C}} \right)^2}}$$

Parallel RLC Circuit :

(3)

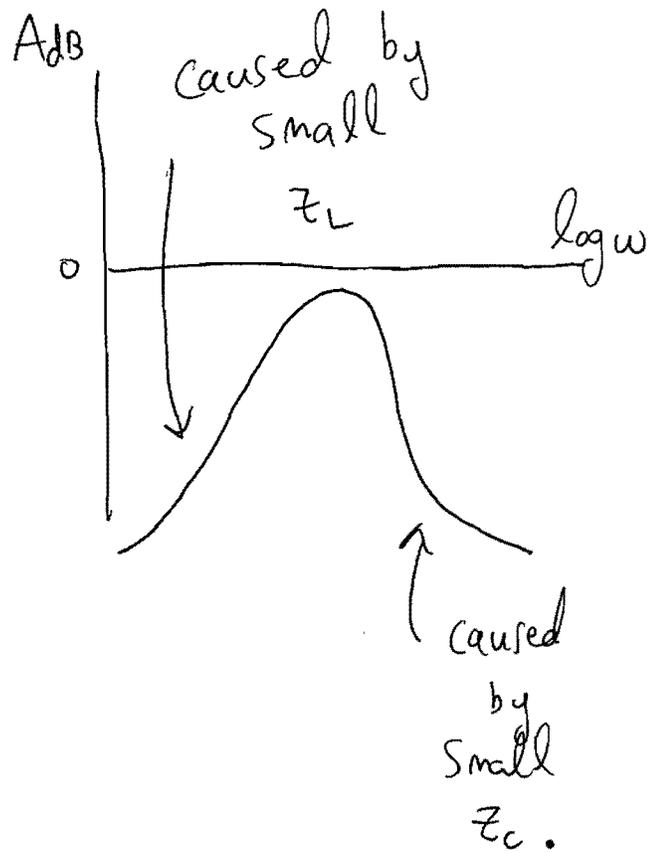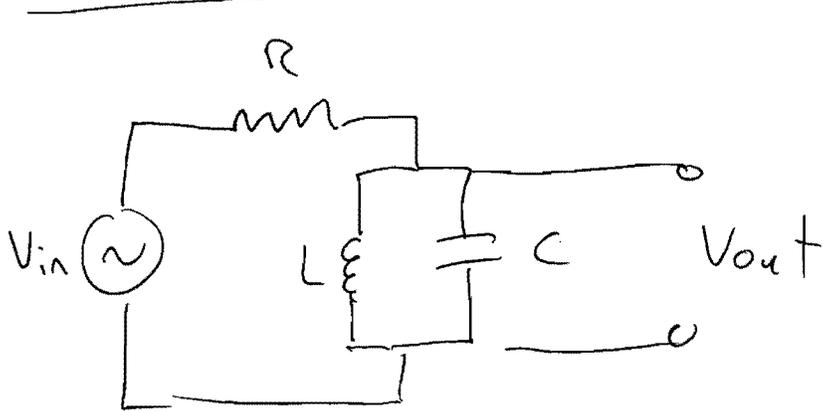

$$A(\omega) = \frac{z_L \parallel z_C}{z_L \parallel z_C + R}$$


$$\frac{1}{z_{||}} = \frac{1}{z_C} + \frac{1}{z_L} = i\omega C + \frac{1}{i\omega L}$$

$$\frac{1}{z_{||}} = i \left(\omega C - \frac{1}{\omega L} \right), \text{ therefore}$$

$$z_{||} = \frac{i}{\left(\frac{1}{\omega L} - \omega C \right)}$$

plug it
in

4

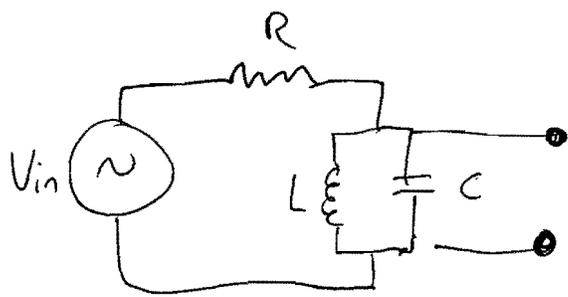

$$A(\omega) = \frac{Z_{||}}{Z_{||} + R}$$

$$A(\omega) = \frac{\frac{1}{\left(\frac{1}{\omega L} - \omega C\right)}}{\frac{i}{\left(\frac{1}{\omega L} - \omega C\right)} + R} = \frac{1}{1 + \frac{R\left(\frac{1}{\omega L} - \omega C\right)}{i}}$$

$$A(\omega) = \frac{1}{1 - i R \left(\frac{1}{\omega L} - \omega C\right)}$$

$$A(\omega) = \frac{e^{i \tan^{-1} \left(R \left(\frac{1}{\omega L} - \omega C\right) \right)}}{\sqrt{1 + R^2 \left(\frac{1}{\omega L} - \omega C\right)^2}}$$