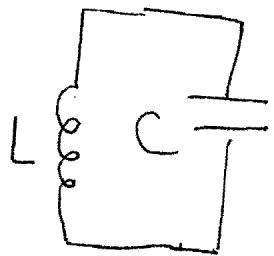


LC - time domain analysis :

①

We know LC circuits oscillate,
lets prove it using conservation
of Energy. $V_L + V_C = 0$



$$L \frac{dI}{dt} + \frac{Q}{C} = 0$$

$$\frac{d^2Q}{dt^2}$$

$$\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q$$


$$Q = Q_0 e^{i\omega t}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$V_C = \frac{Q_0}{C} e^{i\omega t}$$

$$V_L = -\omega^2 L e^{i\omega t}$$

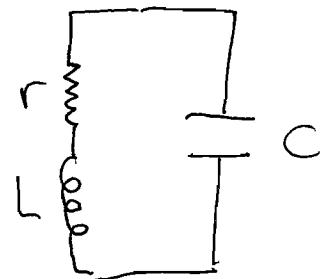The previous equations are true, but we always see loss in our systems due to resistance. (2)



$$V_r + V_L + V_C = 0$$

$$Ir + \frac{LdI}{dt} + \frac{Q}{C} = 0$$

$$r \frac{dQ}{dt} + L \frac{d^2Q}{dt^2} + \frac{Q}{C} = 0$$

rearrange ...

$$\ddot{Q} + \frac{r}{L} \dot{Q} + \frac{Q}{LC} = 0 \quad \left(\dot{Q} = \frac{dQ}{dt} \right)$$

Solve using a root method

Assume $Q(t) = e^{\alpha t}$, plug this in along w/ the correct derivatives and solve for α .

$$\ddot{Q} + \frac{r}{L} \dot{Q} + \frac{Q}{LC} = 0$$

(3)

Ansatz: $Q(t) = e^{\alpha t}$

$$\alpha^2 e^{\alpha t} + \frac{r}{L} \alpha e^{\alpha t} + \frac{e^{\alpha t}}{LC} = 0$$

or

$$\alpha^2 + \frac{r}{L} \alpha + \frac{1}{LC} = 0$$

Solve for α w/ quadratic formula.

$$\alpha = \frac{-\frac{r}{L} \pm \sqrt{\left(\frac{r}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$Q(t) = e^{\alpha t}$$

Check:

when $r \rightarrow 0$ $\alpha = \frac{i}{\sqrt{LC}}$, which

matches our first result.

(4)

when $r \rightarrow \infty$ decay becomes dominant and $Q = e^{-\frac{r}{L}t}$.

The point at which oscillation is no longer seen is found by looking at when α ceases to be complex, when

$$\frac{r}{L} > \frac{2}{\sqrt{LC}} \text{ no more}$$

ringing occurs.