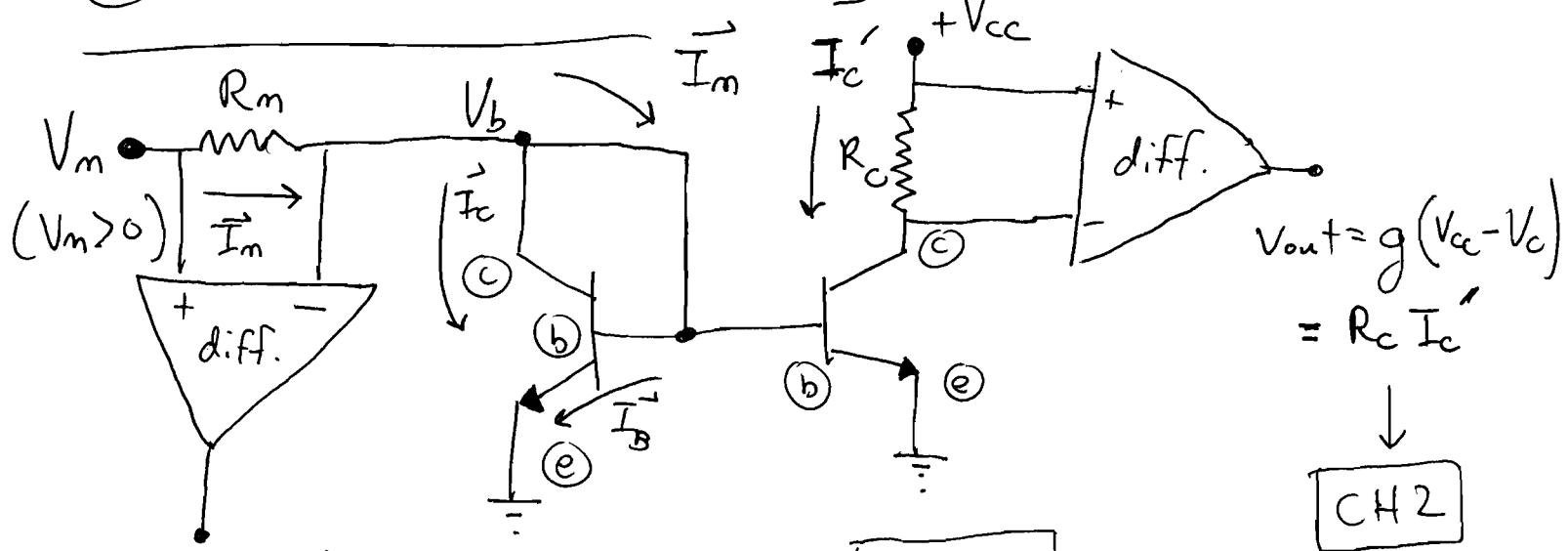


# Current Mirror



$$V_{out} = g(V_m - V_b) = I_m R_m = \boxed{CH1}$$

Start with two npn transistors back-to-back as shown above.

In the left transistor

$$\vec{I}_m = \vec{I}_{total} = \vec{I}_c + \vec{I}_B = \beta I_B + I_B$$

also.  $I_m = \frac{V_m - V_b}{R_m}$ , therefore

$$I_m = \frac{V_m - V_b}{R_m} = (\beta + 1) I_B, \text{ and}$$

remember then  $I_B = I_{\text{Diode}}$

1


due to the current moving through the b-e pn junction.

$$I_B = I_0 (e^{\alpha V_B} - 1) \quad \text{where } \alpha = \frac{e}{k_B T}$$

and,

$$\frac{V_m - V_B}{R_m} = (\beta + 1) I_0 (e^{\alpha V_B} - 1)$$

Solve graphically for  $V_B$

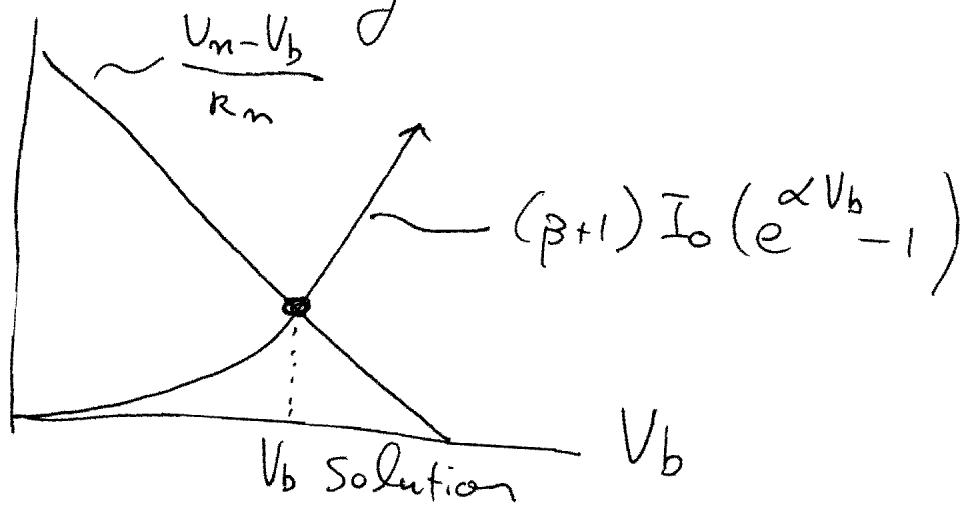


Goal: As  $V_m$  is adjusted both  $I_0$  and  $I_c'$  should have a linear response to the given applied potential. ②

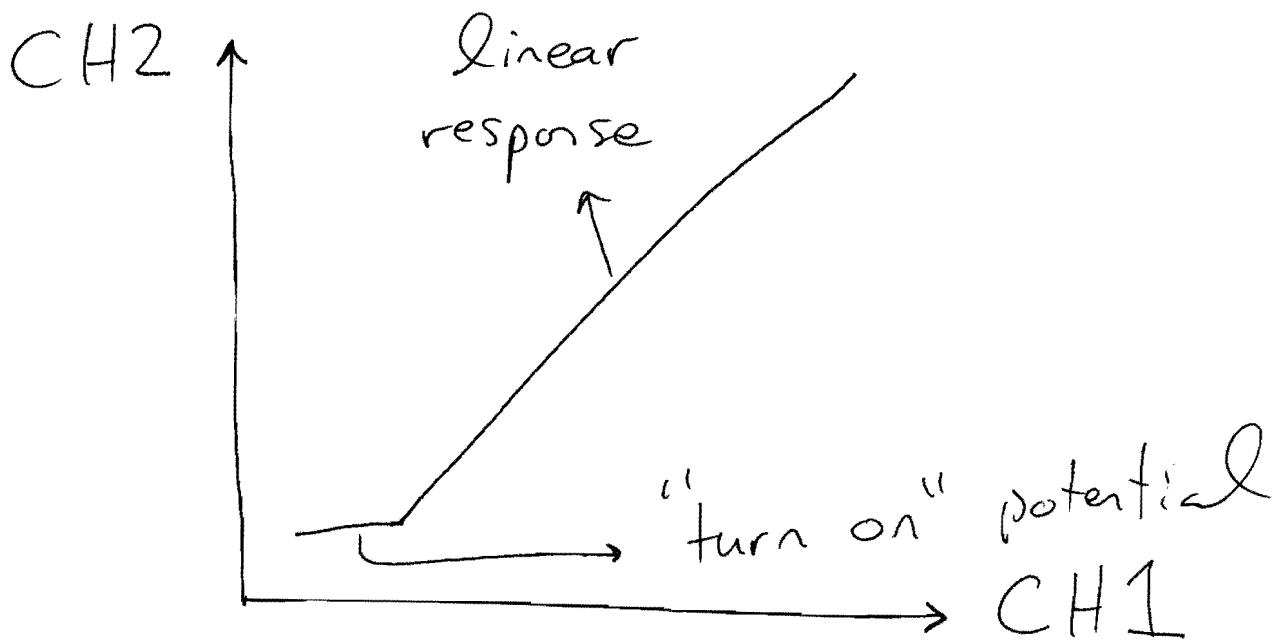
## Xg-mode data :

$$CH1 = V_m - V_b \text{ (drop across } R_m)$$

$$CH2 = g(V_{cc} - V_c) \text{ (drop across } R_c)$$



## Self-Biased Amplifier :

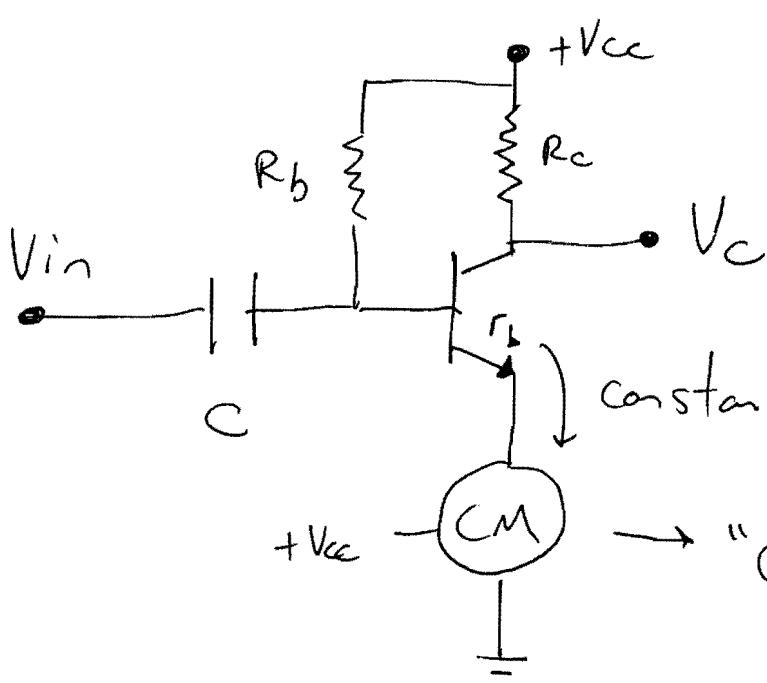


$$\frac{V_{cc} - V_c}{R_c} = I_c$$

constant current

"Current Mirror"

(3)

Remark 5 :

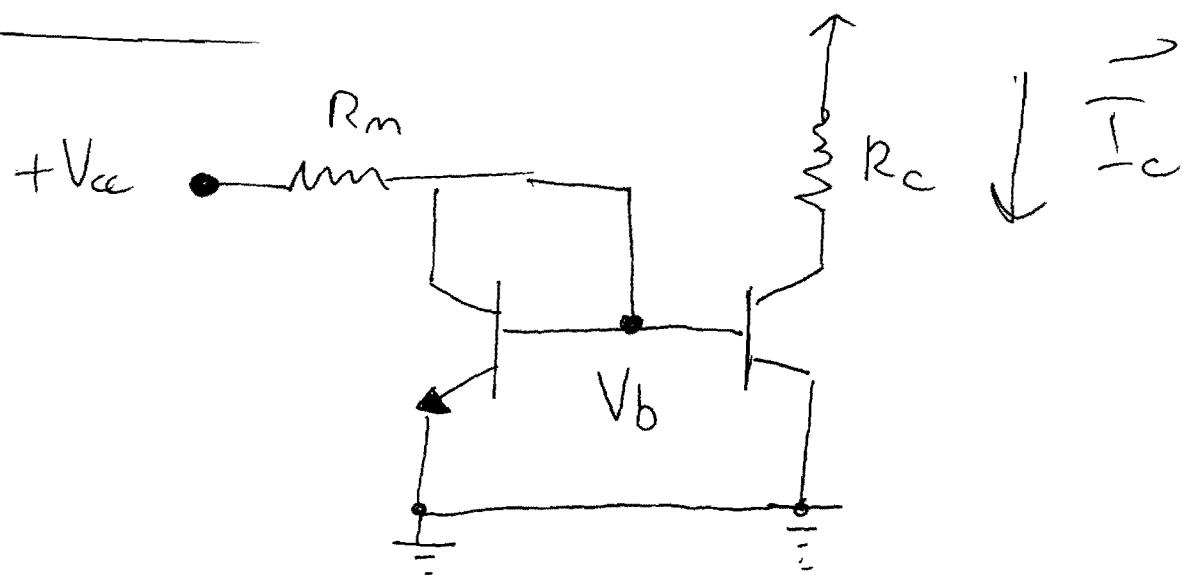

The whole point of the current mirror is to establish a constant  $V_b$  (shown on page ②), this constant  $V_b$  creates a constant  $\bar{I}_c$ . Because  $\bar{I}_c$  is held constant any resistor (or circuit) will adjust its potential drop to maintain constant current.

3A

Refer to Self Biased amplifier  
Circuit diagram :

Conditions :

(A) Want  $V_C = V_{CC}/2$

(B)  $\frac{V_{CC}/2}{R_C} = I_m$

(C)  $\frac{V_{CC}}{R_b} > I_B = \frac{I_m}{\beta}$


(D)  $\left( \frac{V_{CC}}{R_b} \sim 10 I_B \right)$

(E)  $I_m \approx 1mA$

Input impedance  $Z_{in} = Z_C + R_b \parallel r_b$

(4)

# Differential Amplifier :

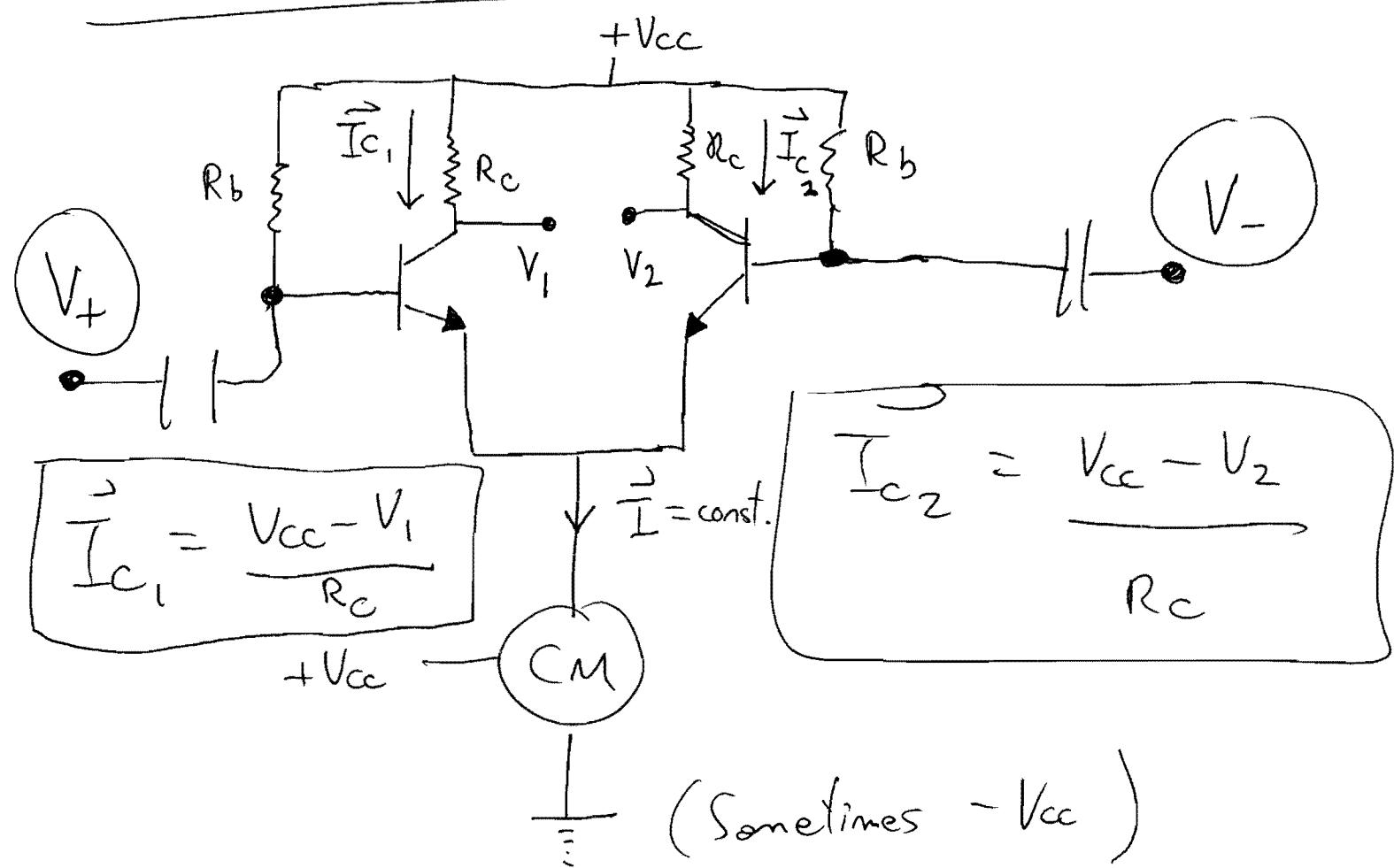

Recall that  $\vec{I} = \text{constant}$

from the current mirror,

and

$$\vec{I}_{C_1} + \vec{I}_{C_2} = \vec{I}$$

Physical reasoning is very important w/ this circuit!!


(5)

## Physical Reasoning :

Consider increasing  $V_+$  input.

- (a) When  $\underline{V_+}$  increases,  $\overline{I_{C_1}}$  increases
- (b) If  $\overline{I_{C_1}}$  increases,  $\underline{V_1}$  decreases
- (c) If  $\overline{I_{C_1}} \uparrow, \overline{I_{C_2}} \downarrow$  \ current  
egn.
- because  $\overline{I_{C_1}} + \overline{I_{C_2}} = \text{constant}$
- (d) If  $\underline{I_{C_2}}$  decreases the  $\underline{V_2}$  increases

Therefore when

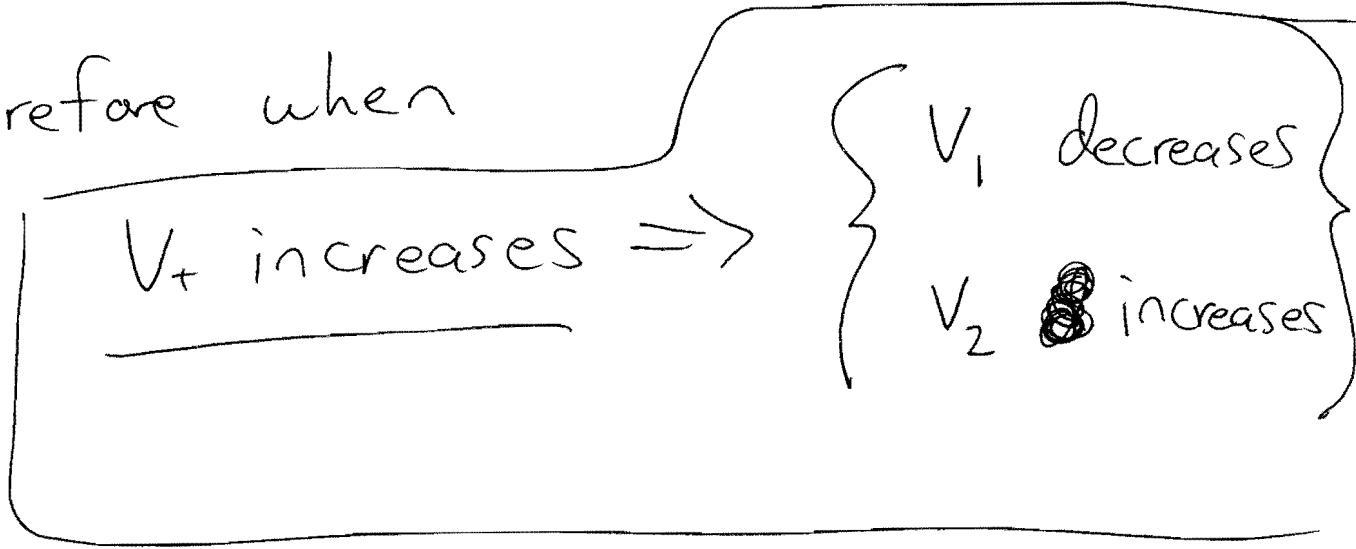

So for  $V_+$   $V_1$  is the inverted output, and  $V_2$  is the non-inverted output.

⑥