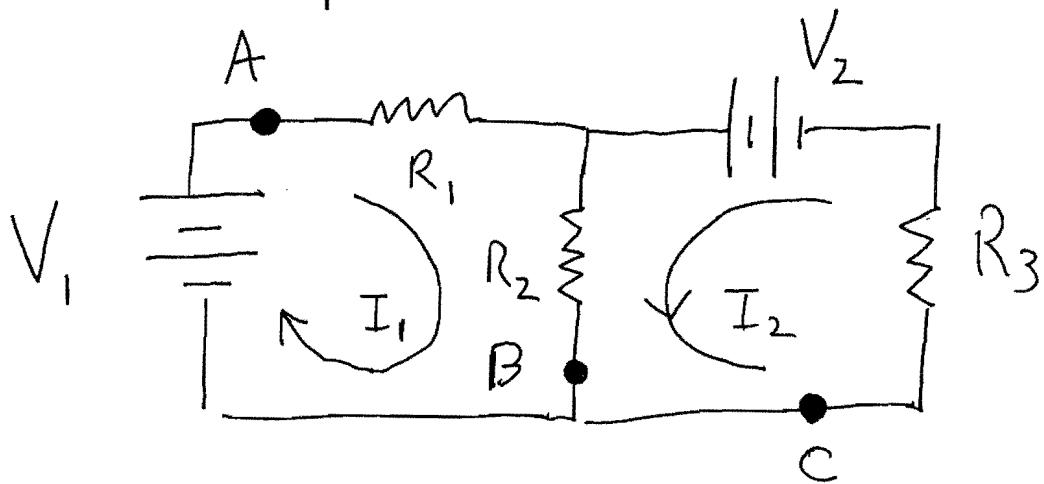


Current Loops :

(1)

Using current loops along with Kirchoff's voltage rules is extremely useful for complex circuits.



Find the current at points A, B, C.


Solution :

Make current loops I_1 and I_2 ,
then use $\sum_{\text{closed loop}} \Phi = 0$ along with

some linear algebra to solve

$$\boxed{I_c = I_2}$$
$$\boxed{I_A = I_1}$$
$$\boxed{I_B = I_1 + I_2}$$

for I_1 and I_2 . Then

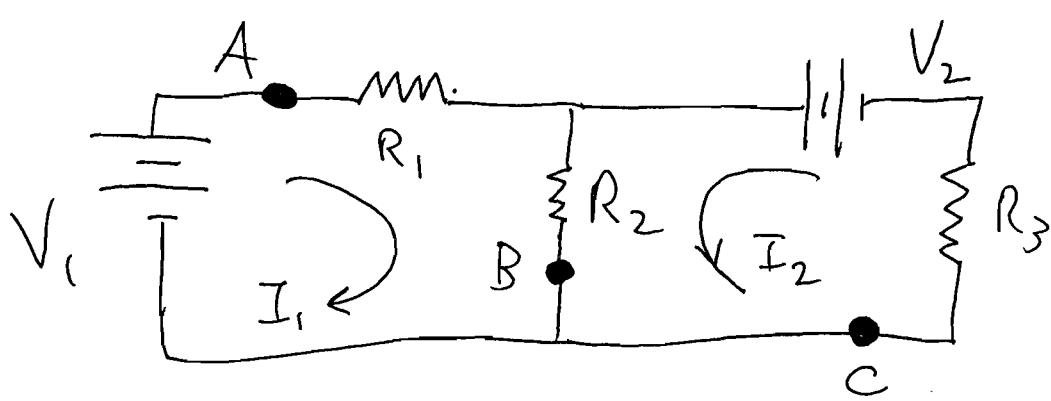

2

$$\begin{aligned} \textcircled{1} \quad V_1 &= I_1 R_1 + (I_1 + I_2) R_2 \\ \textcircled{2} \quad V_2 &= (I_1 + I_2) R_2 + I_2 R_3 \end{aligned} \quad \left. \begin{array}{l} \sum \mathcal{E} = 0 \\ \text{closed loop} \end{array} \right\}$$

Matrix equation :

$$\begin{pmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

Row Reduce matrix to solve
for I_1, I_2 . Remember the

Solution is :

$$I_A = I_1$$

$$I_B = I_1 + I_2$$

$$I_C = I_2$$