

$$\textcircled{1} \quad \frac{I}{A} = \frac{e^2 n \Delta t}{m} E = \sigma E \quad \text{for alum: } M = 0.027 \text{ kg/mole}$$

$$\rho = 2.7 \times 10^3 \text{ kg/m}^3$$

$$G = 3.6 \times 10^7$$

$$n = \left(\frac{3 e^-}{\text{atom}} \right) \left(6.02 \times 10^{23} \frac{\text{atoms}}{\text{mole}} \right) \left(\frac{1 \text{ mole}}{0.027 \text{ kg}} \right) \left(2.7 \times 10^3 \frac{\text{kg}}{\text{m}^3} \right) = 1.8 \times 10^{28} \frac{e^-}{\text{m}^3}$$

$$\Delta t = \frac{\sigma m}{e^2 n} = \frac{(3.6 \times 10^7)(9.1 \times 10^{-31})}{(1.6 \times 10^{-19} \text{ C})(1.8 \times 10^{28} \text{ e}^-/\text{m}^3)}$$

$$= 7.1 \times 10^{-15} \text{ s}$$

assume a typical thermal speed of 10^6 m/s

$$d = v \Delta t = 7.1 \times 10^{-9} \text{ m}$$

$$\text{atomic density} \sim 6 \times 10^{28} \text{ atoms/m}^3 \Rightarrow \text{atomic spacing} = (6 \times 10^{28})^{-1/3}$$

$$= 2.5 \times 10^{-10} \text{ m}$$

$$d = \frac{7.1 \times 10^{-9} \text{ m}}{2.5 \times 10^{-10} \text{ m}} \approx 28 \text{ atoms}$$


- $\textcircled{2}$ (a) The 12-V battery is more successful pushing current counterclockwise than the 8-V battery is pushing current clockwise. So the current flows from B to A.
- (b) The 12-V battery is doing positive work on the flowing charges. The flowing charges do work on the 8-V battery, so the 8-V battery is doing negative work.
- (c) Current flows from B to A, $\Rightarrow V_B > V_A$.

- $\textcircled{3}$ Assume current flows counterclockwise. Applying the loop rule starting from Q:

$$+150 \text{ V} - I(2.0 \Omega) - 50 \text{ V} - I(3.0 \Omega) = 0$$

$$I = \frac{150 \text{ V} - 50 \text{ V}}{5 \Omega} = 20 \text{ A}$$
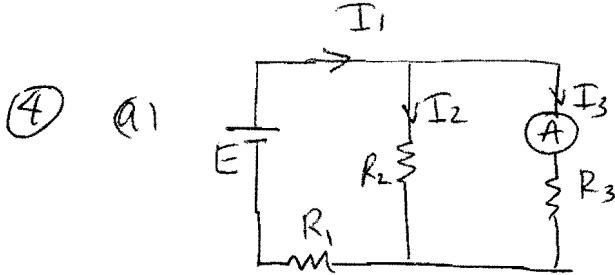
$$V_Q = V_p - 50 \text{ V} - I(3.0 \Omega) = -10 \text{ V}$$



Junction rule: $I_1 = I_2 + I_3$
 Loop rule: $E - I_2 R_2 - I_1 R_1 = 0$
 $- I_3 R_3 + I_2 R_2 = 0$

$$E - I_2 R_2 - I_1 R_1 = 0$$


$$E - I_2 R_2 - (I_2 + I_3) R_1 = 0$$

$$E - I_2 (R_2 + R_1) - I_3 R_1 = 0$$

$$E - I_3 \left(\frac{R_3}{R_2} \right) (R_2 + R_1) - I_3 R_1 = 0$$

$$I_3 = \frac{\frac{E}{R_2}}{\frac{R_3}{R_2} (R_2 + R_1) + R_1} = \frac{R_2 E}{R_3 R_2 + R_3 R_1 + R_2 R_1}$$
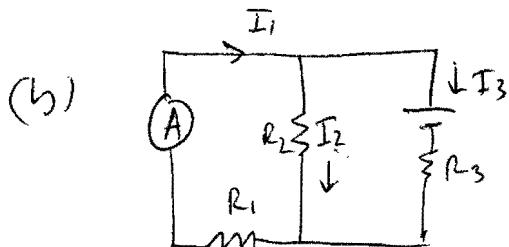
$$= \frac{(4\text{A})(50\text{V})}{(6)(4) + (6)(2) + (4)(2)} = 0.45\text{A}$$



$$I_1 = I_2 + I_3$$


$$-I_2 R_2 - I_1 R_1 = 0$$

$$-E - I_3 R_3 + I_2 R_2 = 0$$

$$-E - (I_1 - I_2) R_3 + I_2 R_2 = 0$$

$$-E - \left(I_1 + I_2 \frac{R_1}{R_2} \right) R_3 - I_1 R_1 \frac{R_1}{R_2} = 0$$
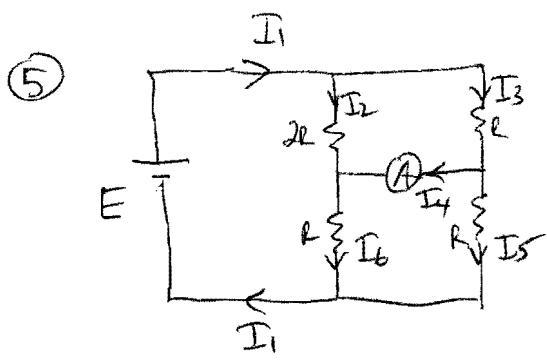
$$I_1 = \frac{-E R_2}{R_2 R_3 + R_3 R_1 + R_2 R_1} = -0.45\text{A}$$



Junctions:

$I_1 = I_2 + I_3$	J_1
$I_3 = I_4 + I_5$	J_2
$I_2 + I_4 = I_6$	J_3
$I_5 + I_6 = I_1$	J_4

Loops:

$E - J_2(2R) - I_6 R = 0$	L_1
$- I_3 R + I_2(2R) = 0$	L_2
$- I_5 R + I_6 R = 0$	L_3

Solve for I_4

$$L_3: I_5 = I_6$$

$$L_2: I_3 = 2I_2$$

$$J_3: I_1 = 2I_6 \Rightarrow I_6 = \frac{1}{2}I_1$$

$$J_1: I_1 = 3I_2 \Rightarrow I_2 = \frac{1}{3}I_1$$

$$L_1: \mathcal{E} - \frac{1}{3}I_1(2R) - \frac{1}{2}I_1R = 0$$

$$\mathcal{E} - \frac{7}{6}I_1R = 0 \Rightarrow I_1 = \frac{6\mathcal{E}}{7R}$$

$$J_3: I_4 = I_6 - I_2 = \frac{1}{2}I_1 - \frac{1}{3}I_1 = \frac{1}{6}I_1$$

$$I_4 = \frac{1}{6} \cdot \frac{6\mathcal{E}}{7R}$$

$$\boxed{I_4 = \frac{\mathcal{E}}{7R}}$$

$$\text{check } I_1 = \frac{6\mathcal{E}}{7R}, I_2 = \frac{2\mathcal{E}}{7R}, I_3 = \frac{4\mathcal{E}}{7R}$$

$$I_6 = \frac{3\mathcal{E}}{7R}, I_5 = \frac{3\mathcal{E}}{7R}$$

(1) $\text{adj} \rightarrow \text{OK}$