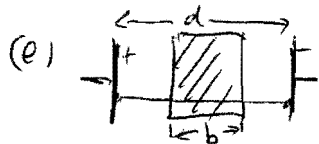


① (a) $C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \text{ pF/m})(0.12 \text{ m}^2)}{0.012 \text{ m}} = 89 \text{ pF}$

(b) $Q = C \Delta V = (89 \times 10^{-12} \text{ F})(120 \text{ V}) = 1.1 \times 10^{-8} \text{ C} = 11 \text{ nC}$
 same after dielectric is inserted.

(c) $E = \frac{Q/A}{\epsilon_0} = \frac{(1.1 \times 10^{-8} \text{ C}) / (0.12 \text{ m}^2)}{8.85 \times 10^{-12} \text{ F/m}} = 10 \text{ kV/m}$

(d) $E' = E/k = 10 \text{ kV/m} / 4.8 = 2.1 \text{ kV/m}$



Integrate along line:

$$\Delta V = E(d-b) + E'(b)$$

$$= (10 \frac{\text{kV}}{\text{m}})(0.008 \text{ m}) + (2.1 \frac{\text{kV}}{\text{m}})(0.004 \text{ m}) = 88 \text{ V}$$

(f) $C = \frac{Q}{\Delta V} = \frac{1.1 \times 10^{-8} \text{ C}}{88 \text{ V}} = 120 \text{ pF}$

(g) Before: $U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(1.1 \times 10^{-8} \text{ C})^2}{89 \times 10^{-12} \text{ F}} = 6.8 \times 10^{-7} \text{ J}$

After: $U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(1.1 \times 10^{-8} \text{ C})^2}{120 \times 10^{-12} \text{ F}} = 5.0 \times 10^{-7} \text{ J}$

$$W_{\text{ext}} = U_f - U_i = -1.8 \times 10^{-7} \text{ J}$$


② (a) Q remain the same. $C = \frac{\epsilon_0 A}{d} \rightarrow C' = \frac{\epsilon_0 A}{2d} = \frac{1}{2} C$

$$\Delta V' = \frac{Q'}{C'} = \frac{Q}{\frac{1}{2} C} = 2 \frac{Q}{C} = 2 \Delta V$$

(b) Initial $U_i = \frac{1}{2} C (\Delta V)^2 = \frac{\epsilon_0 A}{2d} (\Delta V)^2$


Final $U_f = \frac{1}{2} C' (\Delta V')^2 = \frac{1}{2} \frac{\epsilon_0 A}{2d} (2\Delta V)^2 = \frac{\epsilon_0 A (\Delta V)^2}{d}$

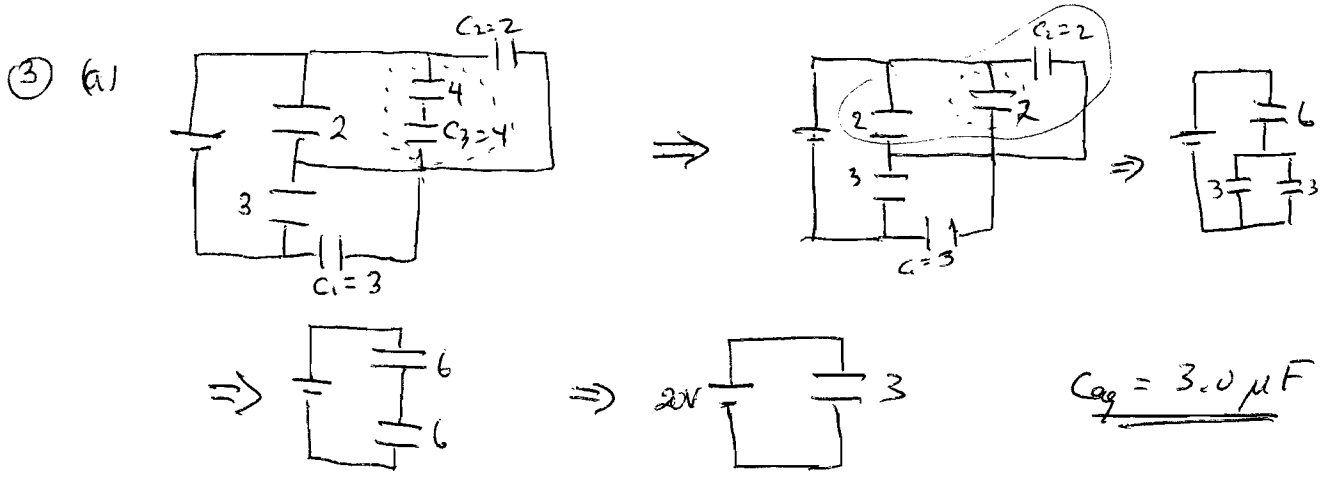(c) $W_{\text{ext}} = U_f - U_i = \frac{\epsilon_0 A (\Delta V)^2}{d} - \frac{\epsilon_0 A (\Delta V)^2}{2d} = \frac{\epsilon_0 A (\Delta V)^2}{2d}$



(b) $Q = C_{eq} \Delta V = C_{eq} \mathcal{E} = (3.0 \mu F)(20V) = 60 \mu C$

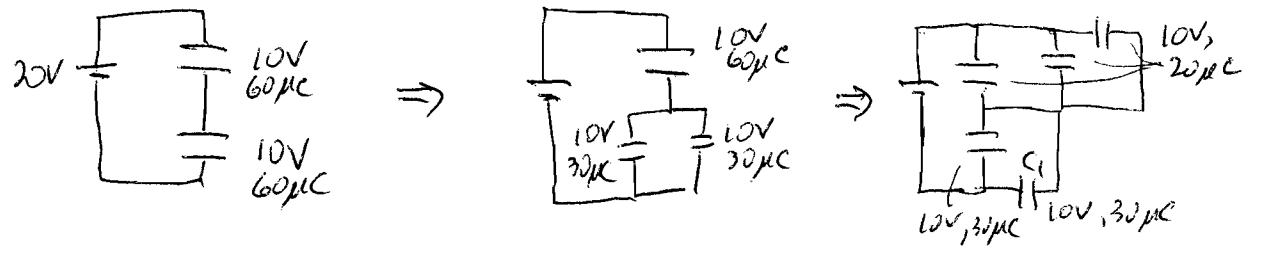(c) Work backwards to find Q and ΔV for each capacitor.



\Rightarrow on C_1 : 10V, 30 μC

(d) on C_2 : 10V, 20 μC

(e) on C_3 : 5V, 20 μC .

④ (a) $\Delta V_c = \mathcal{E} (1 - e^{-t/RC}) \Rightarrow e^{-t/RC} = 1 - \frac{\Delta V_c}{\mathcal{E}}$

$-\frac{t}{RC} = \ln(1 - \frac{\Delta V_c}{\mathcal{E}})$

$RC = \frac{-t}{\ln(1 - \frac{\Delta V_c}{\mathcal{E}})} = - \frac{1.3 \mu s}{\ln(1 - \frac{5V}{12V})} = 2.4 \mu s$


(b) $C = \frac{2.41 \mu s}{R} = \frac{2.41 \mu s}{15,000 \Omega} = 161 pF$

5. The charge on cap in RC circuit is

$$Q(t) = EC(1 - e^{-t/RC})$$

$$\Delta V_c(t) = C \cdot Q(t) = E(1 - e^{-t/RC})$$

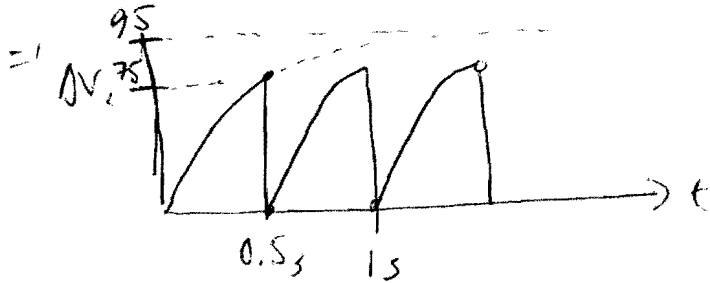at 75 volts, lamp fires & uses all charge
(i.e. comere flash)



$$\Rightarrow \Delta V_c(0.5s) = 75V = 95V(1 - e^{-t/RC})$$

$$\text{or } V_0 = E(1 - e^{-t/RC}) \quad \text{at } t = 0.5s$$

$$\Rightarrow e^{-t/RC} = 1 - \frac{V_0}{E}$$

$$\frac{t}{RC} = -\ln\left(1 - \frac{V_0}{E}\right)$$

$$R = \frac{t}{C} \frac{1}{-\ln\left(1 - \frac{V_0}{E}\right)}$$

$$= \frac{0.5s}{0.15\mu F} \frac{1}{-\ln\left(1 - \frac{75}{95}\right)}$$

$$= \frac{0.5s}{0.15\mu F} \frac{1}{\ln\frac{95}{20}}$$

$$R = 2.14 \times 10^6 \Omega$$