

Homework 3

Due Wednesday 12/4 in class

- 1) Calculate by hand using paper and pencil (no computers) the Fourier transform of the LRC impulse response function $\chi(t)$:

$$\chi(t) = \frac{1}{L} e^{-\beta t} \left[\cos \omega_1 t - \frac{\beta}{\omega_1} \sin \omega_1 t \right] \theta(t),$$

and show that it is equal to the admittance ($1/Z(\omega)$) (modulo a factor of $\sqrt{2\pi}$).

- 2) Show that, in the case of very small damping ($\beta \ll \omega_0$) and frequencies close to resonance, the real part of the complex admittance can be written simply as

$$\operatorname{Re} \left(\frac{1}{Z(\omega)} \right) = \frac{1}{R} L(\omega),$$

where $L(\omega)$ is a Lorentzian function that has the form

$$L(\omega) = \frac{\left(\frac{\Delta\omega}{2} \right)^2}{(\omega - \omega_0)^2 + \left(\frac{\Delta\omega}{2} \right)^2}.$$

The Lorentzian is centered at ω_0 and has a full-width-half-maximum (FWHM) of $\Delta\omega$.

Determine the width $\Delta\omega$ in terms of the defined circuit parameters. Plot this new approximate expression with the exact expression for comparison.

- 3) Show that, given the same conditions as in (2) above, the quality factor can be expressed as

$$Q = \frac{\omega_0}{\Delta\omega}.$$