

PH421 Clicker questions





Series LRC Circuit

Which admittance plot $|Y(\omega)|$ corresponds to which free decay plot $I(t)$?

(All plots scaled to 1 at maximum value)



(A) i \leftrightarrow 1, ii \leftrightarrow 2

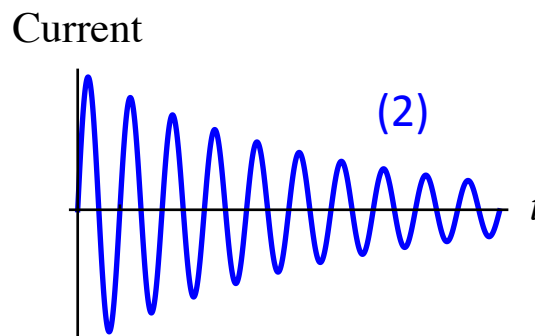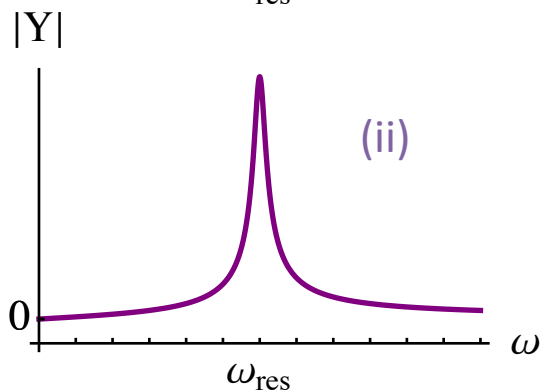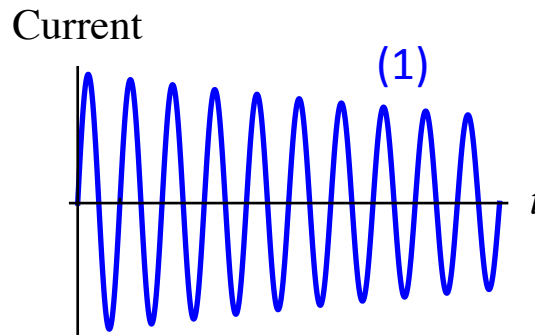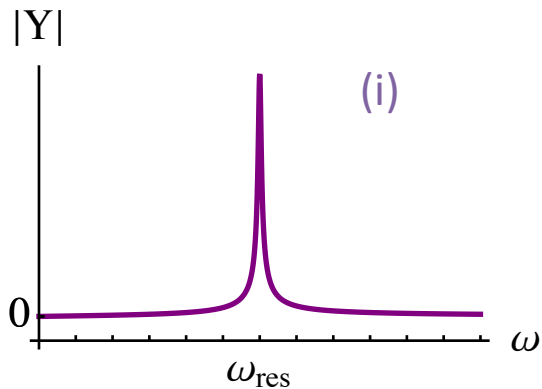(B) i \leftrightarrow 2, ii \leftrightarrow 1




Series LRC Circuit


If the admittance $|Y(\omega)|$ and the phase ϕ_1 response of a series LCR circuit are as given on the left below, then which oscilloscope trace on the right corresponds a circuit driven below resonance? Red is drive voltage, blue is current, represented by V_R .

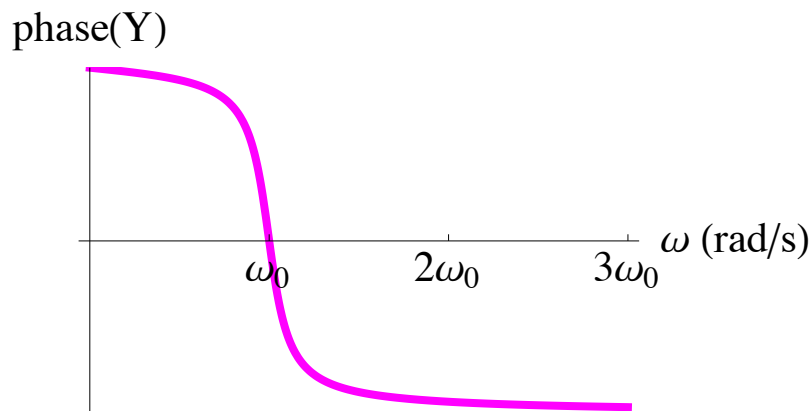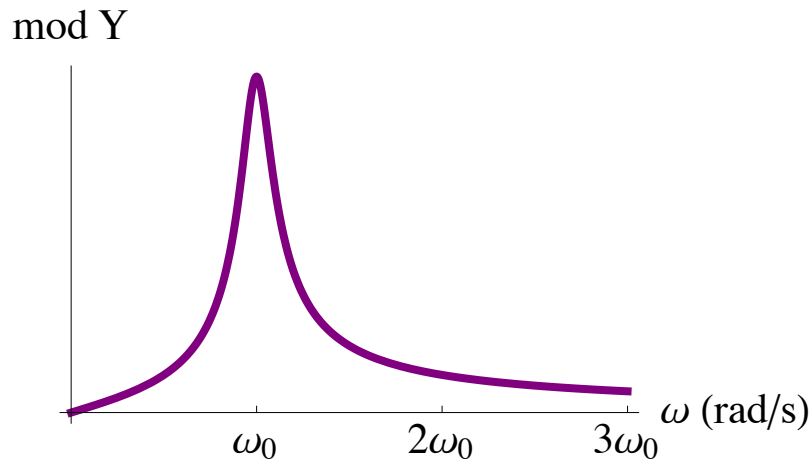


(A)

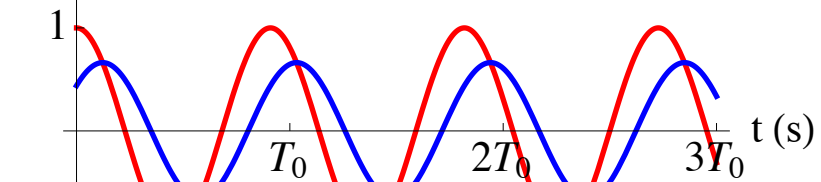


(B)

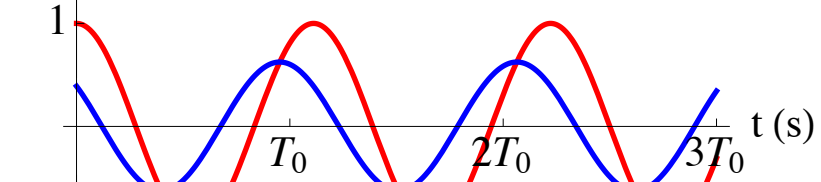


(C)

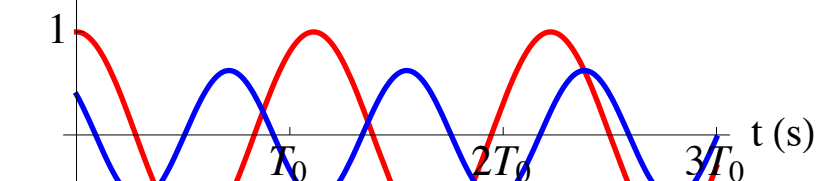


(D)

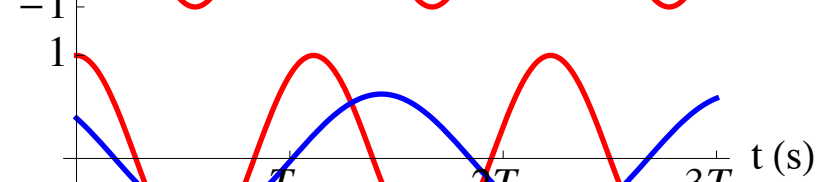


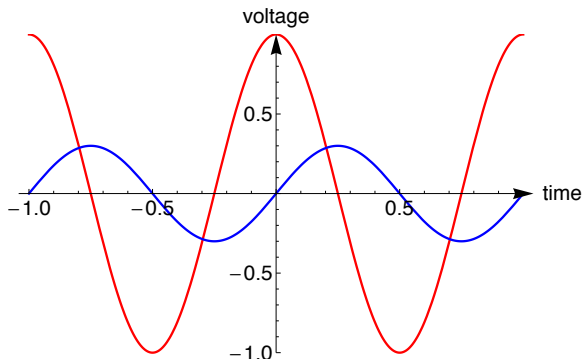

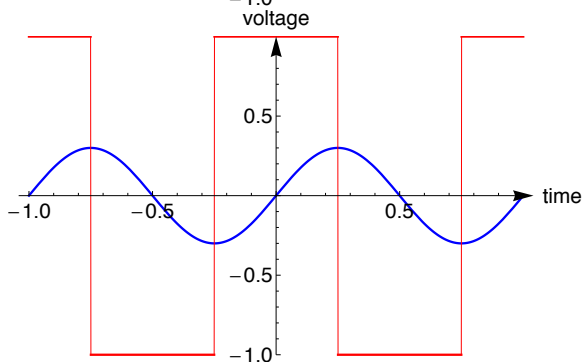
← Suppose that, if you apply a (red) sinusoidal voltage across a series LRC circuit, you measure the (blue) voltage response across the resistor.



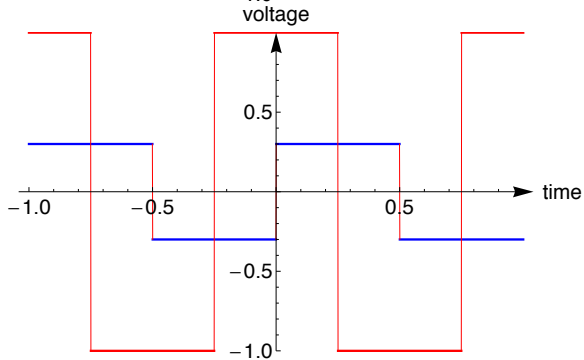← Now, if you now apply a (red) square-wave voltage with the same period to the same circuit, and you measure the (blue) voltage response across the resistor, will you get this?




← Or this?

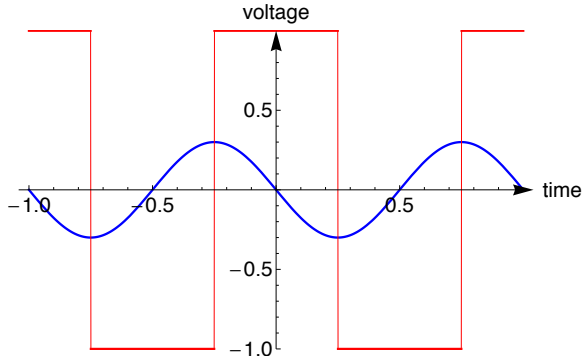


← Or this?


Or something else?

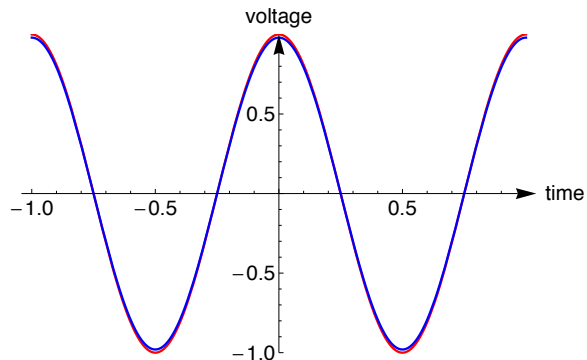

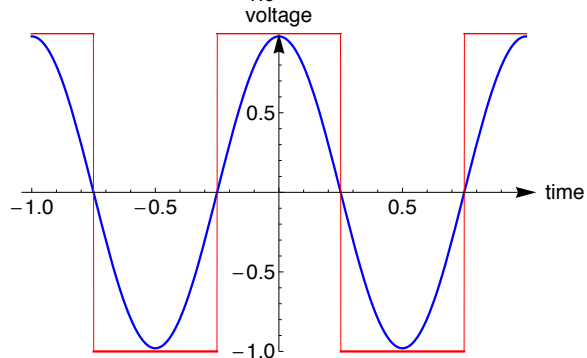
← Suppose that, if you apply a (red) sinusoidal voltage across a series LRC circuit, you measure the (blue) voltage response across the resistor.



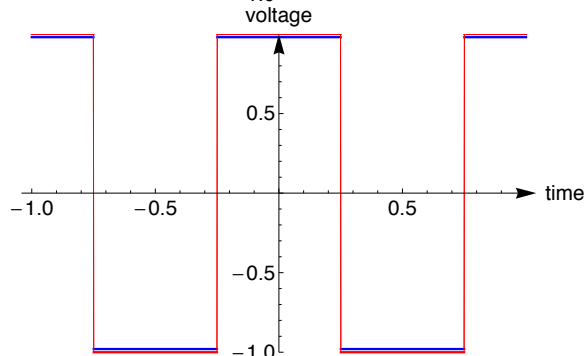← Now, if you now apply a (red) square-wave voltage at the same frequency the same circuit, and you measure the (blue) voltage response across the resistor, will you get this



← Or this?

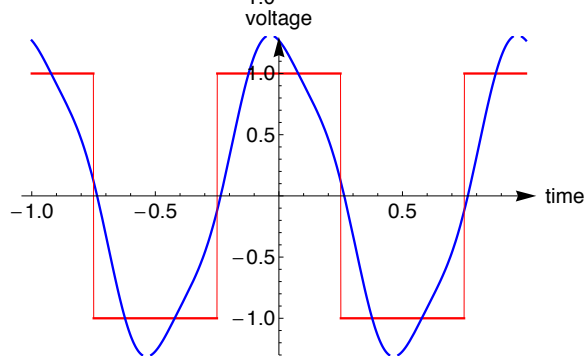


← Or this?

Or something else?

Response functions

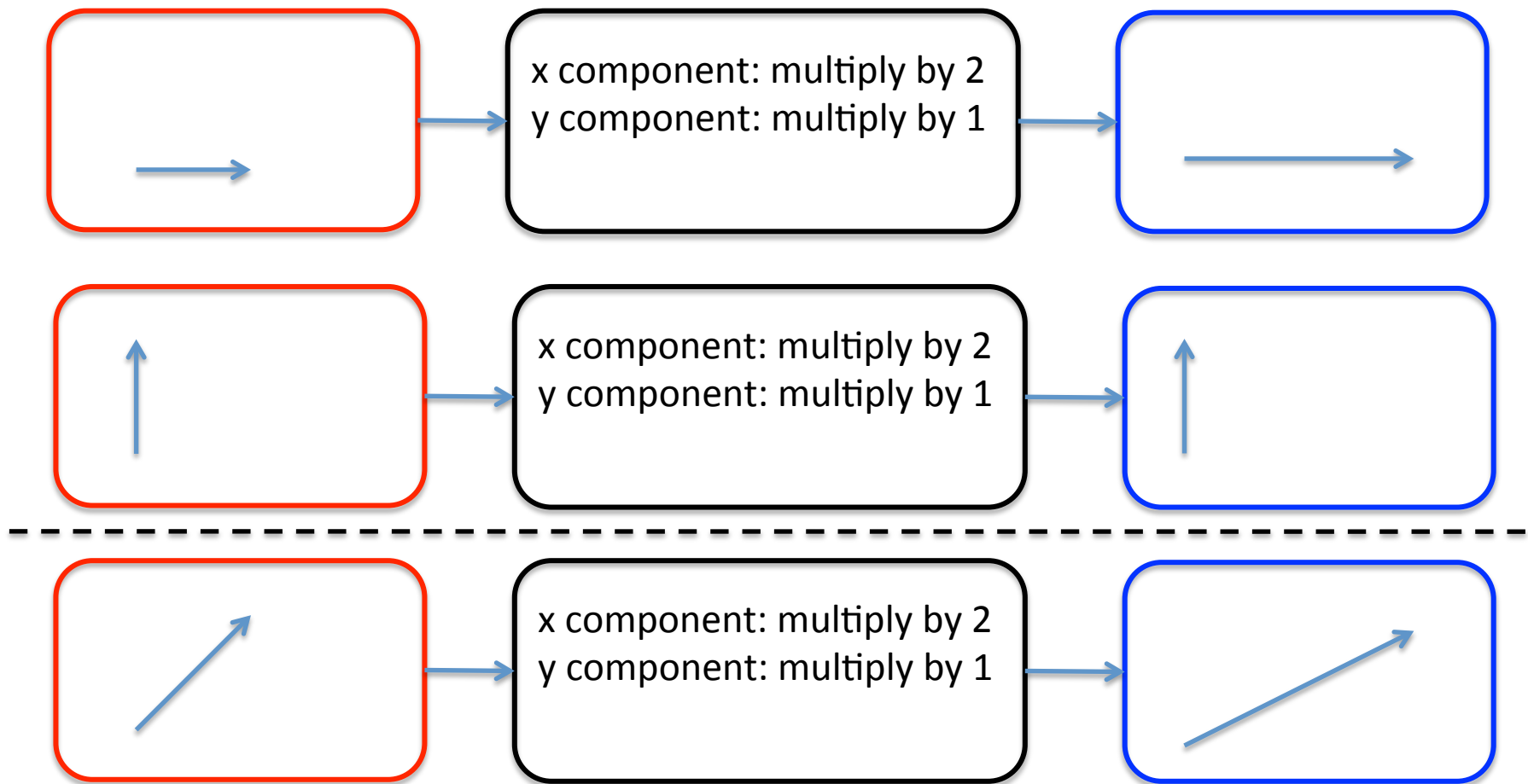A mathematical function can be considered a box that receives **input** (a drive), and produces **output** (a response). Here the box tells how to treat each component of a 2-d vector.









Response functions

A circuit can be considered a box that receives **input** (a drive), and produces **output** (a response). Again the box tells how to treat **each component**. We have to know what the components are.

$$\ddot{q} + 2\beta\dot{q} + \omega_0^2 q = V_0 e^{i\omega t}$$
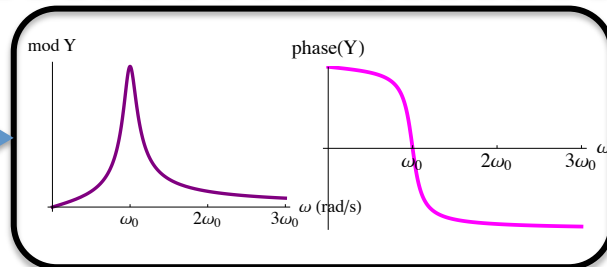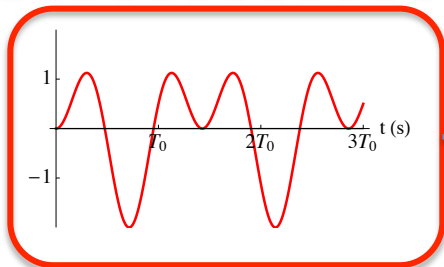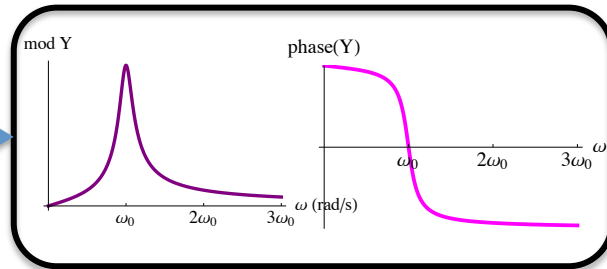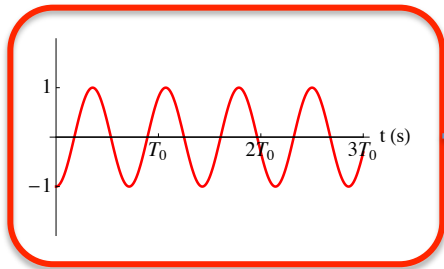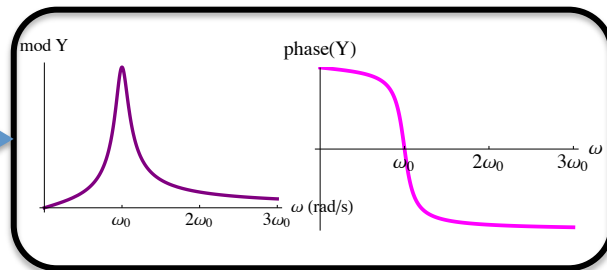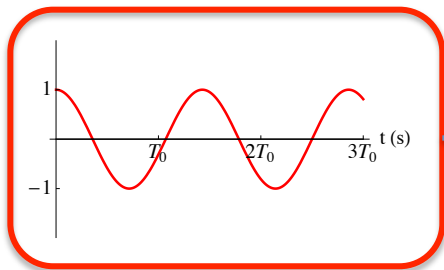
$$\ddot{I} + 2\beta\dot{I} + \omega_0^2 I = i\omega V_0 e^{i\omega t}$$



Response functions

A circuit can be considered a box that receives **input** (a drive), and produces **output** (a response). Again the box tells how to treat **each component**. We have to know what the components are.

$$\ddot{q} + 2\beta\dot{q} + \omega_0^2 q = V_0 e^{i\omega t}$$

$$\ddot{I} + 2\beta\dot{I} + \omega_0^2 I = i\omega V_0 e^{i\omega t}$$

