

RC Circuits :

①

With the introduction of the capacitor comes unique electrical response as a function of time.

Time Domain Analysis :


Technique = Kirchhoff's energy conservation

$$\Rightarrow \sum_{\text{closed loop}} \Phi = 0$$

Solve resulting differential equation.

RC Discharging :

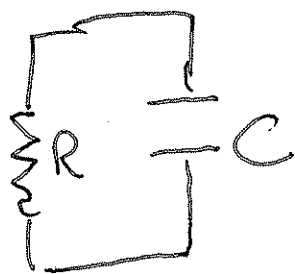Consider a fully charged capacitor / close switch...



$$Q = CV \text{ or } C_1 V + C_2 V + \dots$$

$$V_R = IR, \quad \frac{Q}{C} = V_C$$

$$\Rightarrow \frac{Q}{C} = IR = R \frac{dQ}{dt} \quad \left(I = \frac{dQ}{dt} \right)$$


losing charge

$$\frac{dQ}{dt} = -\frac{1}{RC} Q$$

$$\Rightarrow \boxed{Q(t) = Q_0 e^{-t/RC}}$$

RC Charging:

(2)

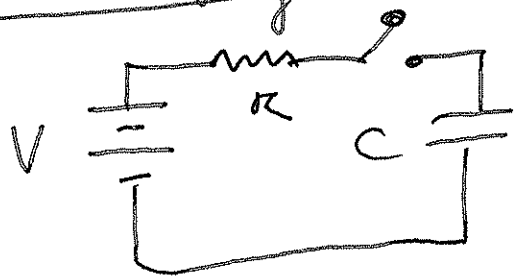


$$\sum \Phi = 0$$

$$V - IR - \frac{Q}{C} = 0$$

$$V - R \frac{dQ}{dt} - \frac{Q}{C} \Rightarrow \frac{dQ}{dt} = \frac{CV - Q}{RC}$$

$$\int_0^Q \frac{dQ'}{Q' - CV} = \int_0^t \frac{-dt}{RC} = -\frac{t}{RC} = \ln(Q' - CV) \Big|_{Q'=0}^{Q'=Q}$$
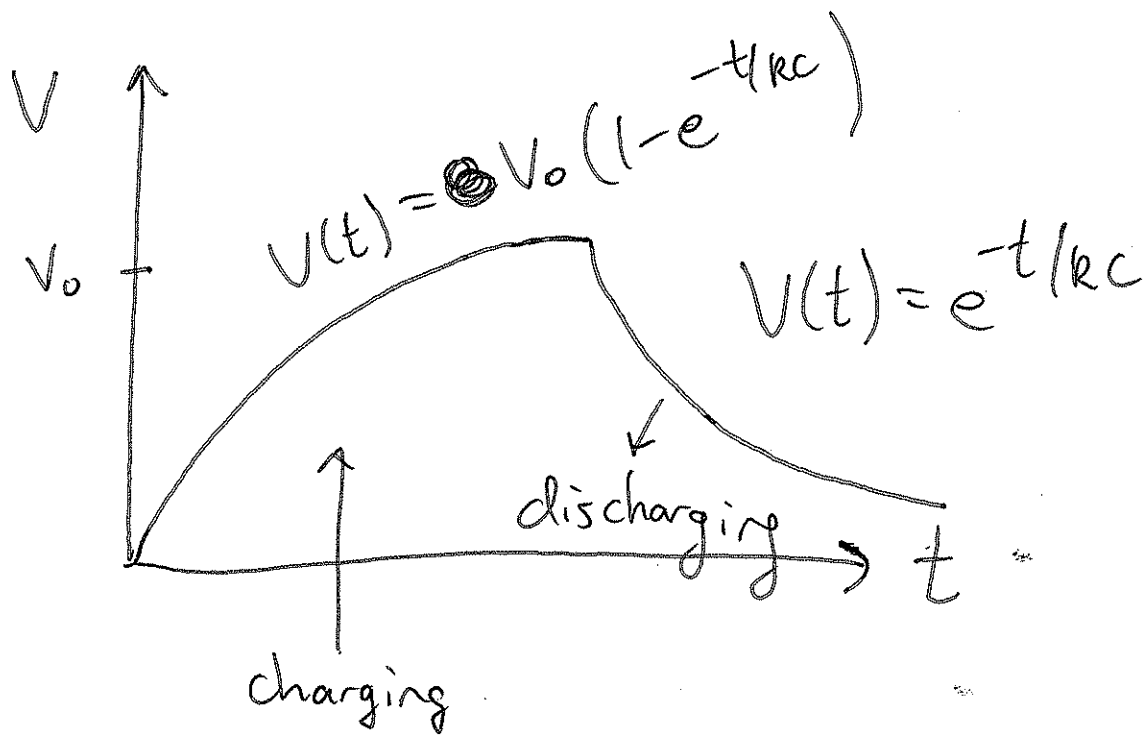
$$\frac{Q - CV}{-CV} = e^{-t/RC} \text{ or } \boxed{Q(t) = CV(1 - e^{-t/RC})}$$




Frequency domain RC

③

Now consider some frequency dependent voltage source. Take for example a sin function (ie. $\sin(\omega t)$) instead of a battery. Frequency dependent response is a fundamental physical property.

Capacitor Impedance : $(Z_c = \frac{1}{i\omega C})$ Explain ...

RC Filter:

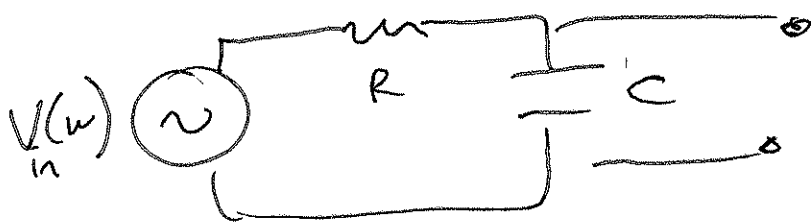


$$V_{out} = \left(\frac{Z_c}{Z_c + R} \right) V_{in}$$

$$\frac{V_{out}}{V_{in}} = A(\omega) = \frac{Z_c}{R + Z_c}$$

$$A(\omega) = \frac{\frac{1}{i\omega C}}{\frac{1}{i\omega C} + R}$$

(Step aside for complex #)

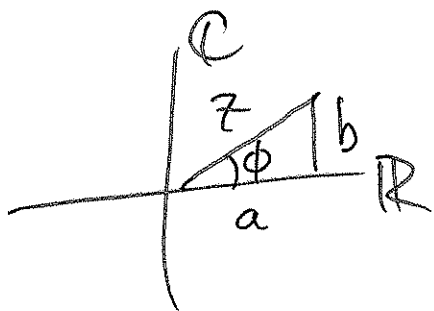

$$z = a + ib$$

(4)

$$|z|^2 = a^2 + b^2$$


$$\cos \phi = \frac{a}{\sqrt{a^2 + b^2}}$$

$$\tan \phi = \frac{b}{a}, \quad \sin \phi = \frac{b}{\sqrt{a^2 + b^2}}$$

$$\frac{a + ib}{\sqrt{a^2 + b^2}} = \cos \phi + i \sin \phi = e^{i\phi}$$

$$a + ib = |z| e^{i\phi}$$
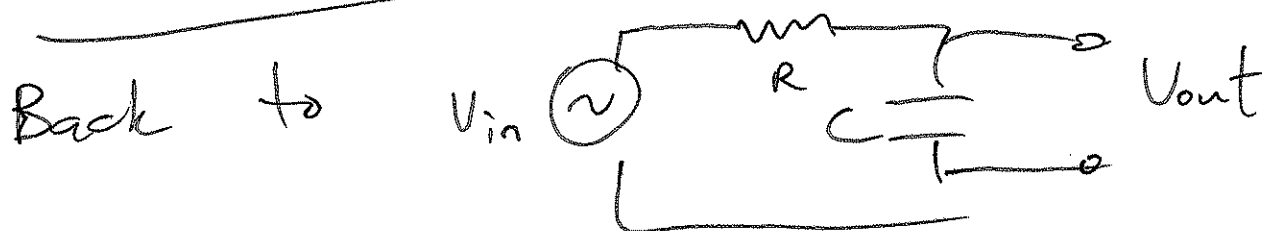
$$\phi = \tan^{-1}\left(\frac{b}{a}\right)$$



$$A(\omega) = \frac{1}{i\omega C + R} = \frac{1}{1 + i\omega RC}$$

$$|A(\omega)| = \frac{e^{-\tan^{-1}(\omega RC)}}{\sqrt{1 + (\omega RC)^2}}$$


$$\text{Phase } \phi = \frac{2\pi\Delta t}{T}$$

Draw

5

Now look @ $|A(\omega)|$ and $\phi(\omega)$ as $\omega \rightarrow 0$ and $\omega \rightarrow \infty$

$$|A(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

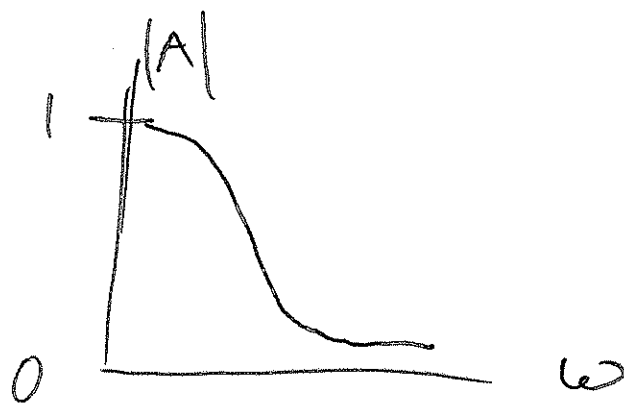

$$\phi = -\tan^{-1}(\omega RC)$$

